

EECS 140: Lab 5 Pre-Lab

# **Implementing a SOP Expression on Prototyping board**

*Morgan Bergen*

**KUID: 3073682**

*Date submitted: 09/27/2023*

**1. What are the three main sections of the prototype board that you soldered in Lab 4.**

The three main sections of the prototype board that we implemented, built, and soldered was as follows,

1. Power Input Circuit Section
2. Switch Circuit Section
3. LED Display Section

**4. How many possible inputs and outputs can you have on the prototype board?**

Because there are 4 input switches there are 16 different possible outputs that the board could have.

The following is a possible truth table demonstrating this fact,

SW5	SW4	SW3	SW2	OUTPUT
0	0	0	0	possible output 1
0	0	0	1	possible output 2
0	0	1	0	possible output 3
0	0	1	1	possible output 4
0	1	0	0	possible output 5
0	1	0	1	possible output 6
0	1	1	0	possible output 7
0	1	1	1	possible output 8
1	0	0	0	possible output 9
1	0	0	1	possible output 10
1	0	1	0	possible output 11
1	0	1	1	possible output 12
1	1	0	0	possible output 13
1	1	0	1	possible output 14
1	1	1	0	possible output 15
1	1	1	1	possible output 16

**5. How would you provide a logic '0' or '1' as input?**

For the input switches - a jumper on the right indicates a 0, a jumper on the left indicates a 1.

There additionally must have to be a supply of power that is connected to the Power input circuit section where the ground and +5 VDC is connected.

**6. How would you monitor the output(component and logic)?**

The way in which you monitor the connect is to visually see if the green LED display is on or off. Because this board is an inverted board a false output would cause the LED to be on and a true output would cause the LED to be off.